













www.knx.org


KNX city

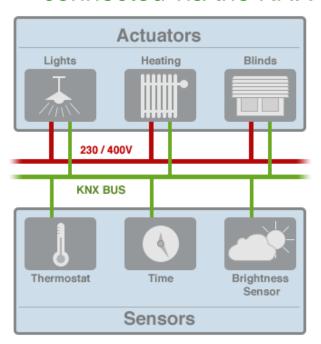Part 1: KNX Introduction



The KNX fieldbus

- KNX is a standardized communication protocol for intelligent buildings
- Sensors, actuators and control systems (e.g. controllers) are connected via the KNX bus



Power cables are only necessary for the actuators


For the KNX bus only a KNX power supply is needed

All KNX devices communicate by telegrams with each other





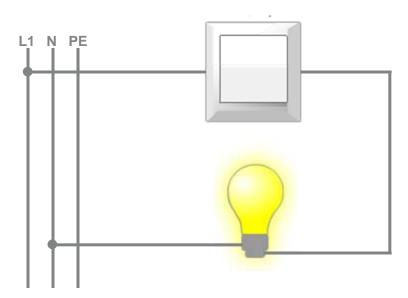
→ In a conventional light power circuit a switch closes the circuit and switches the light on







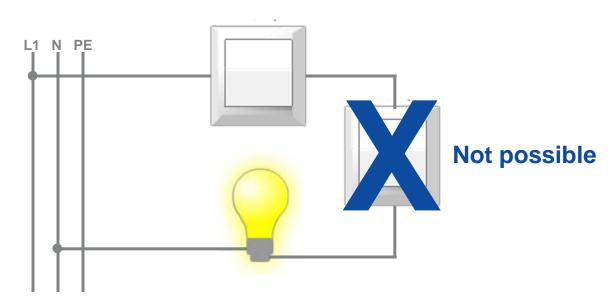→ How to switch the same lamp in a circuit with two switches?



- → A light power circuit with two or three switches can be only implemented with special circuits
- → For more than three switches relays must be used.



KNX transmission media



Twisted Pair (TP)



Powerline (PL)



Radio Frequency (RF)



Infrarot (IR)




Ethernet (IP)



KNX topology

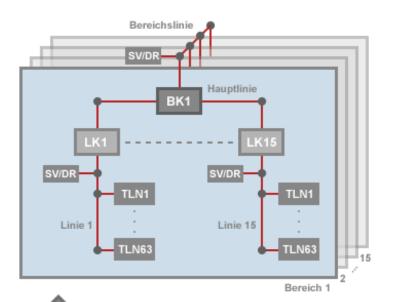- Up to 64 devices in a line
- Up to 15 lines in an area
- Up to 15 areas in a backbone



- BK = Bereichskoppler LK = Linienkoppler TLN = Teilnehmer
- SV/DR = Spannungsversorgung mit Drossel

- Lines or areas may be coupled with TP or IP
- KNX participants need a unique address
- Each line requires a KNX power supply



Programming of KNX systems

- Applications and functions need to be programmed with the ETS
- The programming needs to be done only one time and will be saved in the KNX devices
- With the ETS, the "virtual" inputs and outputs of the devices, called communication objects linked by group addresses








→ The most low voltage and KNX devices will be plugged on a DIN rail







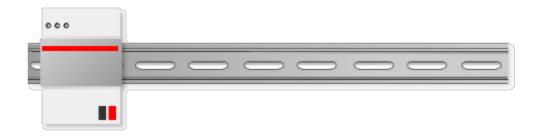
→ A KNX power supply builds the KNX fieldbus and offers the medium Twisted Pair (TP)







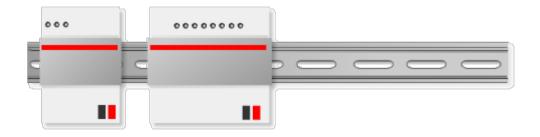→ The switch itself is provided by a KNX switching actuator






Functionality of a KNX fieldbus

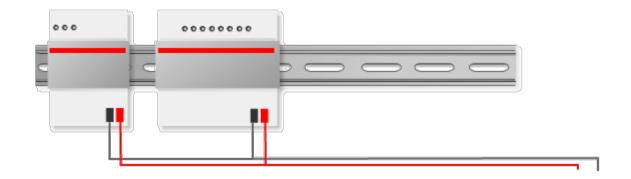Example: Conventional light power circuit


→ All KNX devices are connected to each other via the KNX TP cable







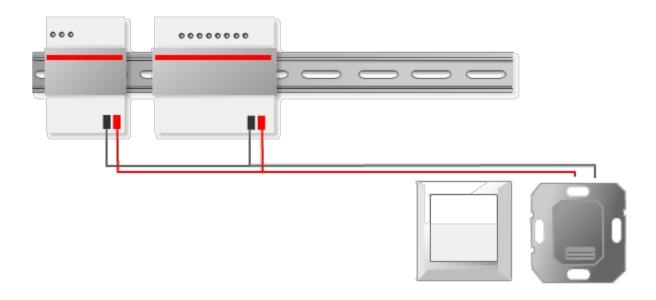
→ A switch including a KNX coupling unit serves as a sensor in order to switch on the light.







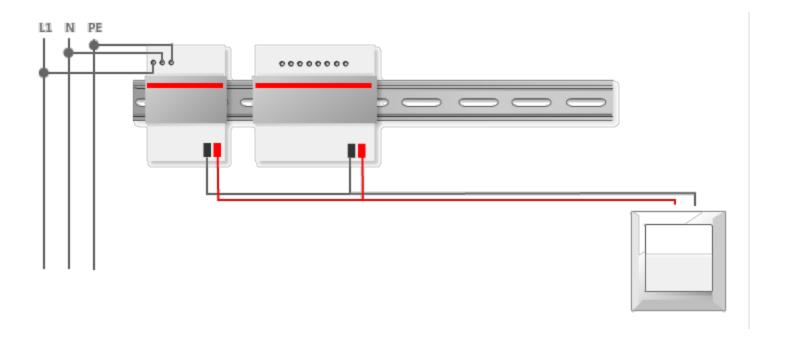
→ The KNX power supply has to be connected to the power







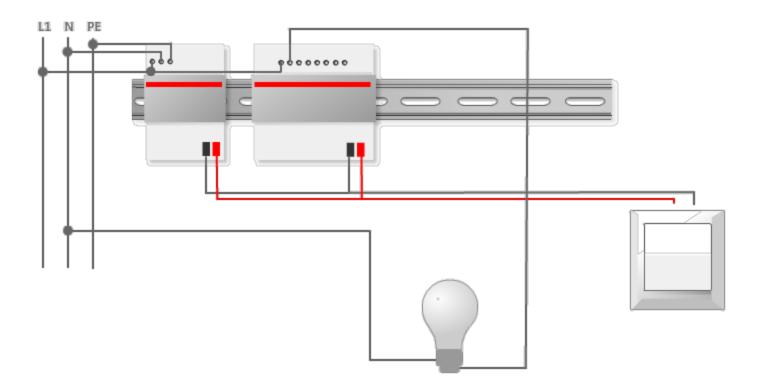
→ The light power circuit has to be wired with the switching actuator







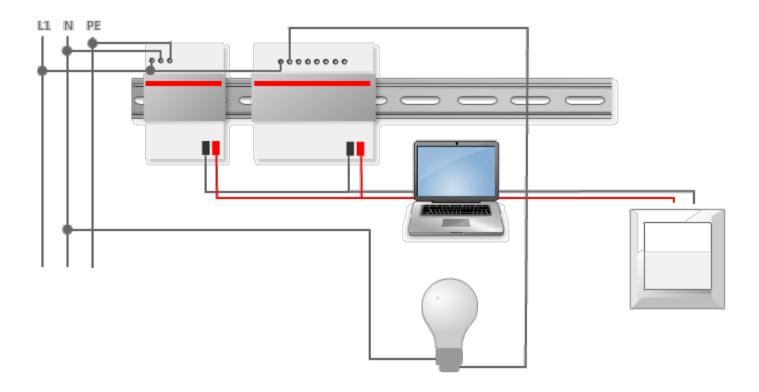→ All KNX devices have to be programmed with the ETS






Functionality of a KNX fieldbus

Example: Conventional light power circuit, programming


Group objects KNX switching actuator



Group objects KNX switch

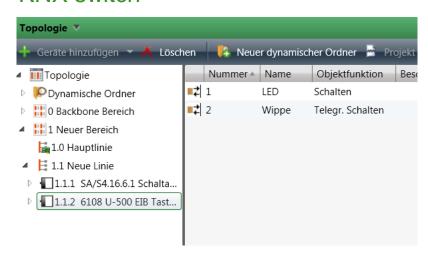


Linking of the group objects

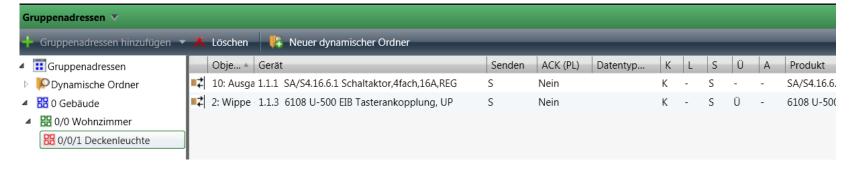





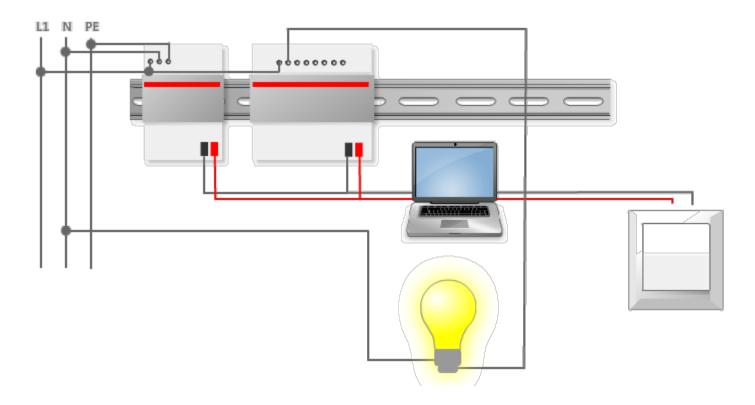→ By pushing the switch, a telegram is sent to the switching actuator, which switches the light on







- Power circuits with many switches for the same lamp can be realized easily
 - → Simplification of the electrical installation
- A switching actuator can switch several power circuits and can control thereby different lamps. In dependence of the programming different light scenes can be realized
 - → More comfort for the user
- A KNX switch represents a sensor. The switching actuator can switch as well in dependence of any other KNX devices, e.g. such as a presence detector.
 - → More energy efficiency



Contact

Lutz Steiner

lutz.steiner@knx.org

KNX Association Brussels

